



# Circuit Design with VHDL

## Chapter 6: Code structure and Composition

**Instructor: Ali Jahanian**



# Outline

- I-CIRCUIT DESIGN

- 2 Code Structure

- 2.1 Fundamental VHDL Units


- 2.2 LIBRARY Declarations

- 2.3 ENTITY

- 2.4 ARCHITECTURE


- 2.5 Introductory Examples

# Fundamental VHDL Units

 

**Figure 2.1**  
Fundamental sections of a basic VHDL code.

# LIBRARY

 

**Figure 2.2**  
Fundamental parts of a LIBRARY.

# LIBRARY Declarations

- To declare a **LIBRARY**

```
LIBRARY library_name;  
USE library_name.package_name.package_parts;
```

**At least three packages, from three different libraries, are usually needed in a design:**

- *ieee.std\_logic\_1164* (from the *ieee* library),
- *standard* (from the *std* library), and
- *work* (*work* library).

# LIBRARY Declarations ...

**specifies a multi-level logic system**

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

LIBRARY std;
USE std.standard.all;

LIBRARY work;
USE work.all;
```

-- A semi-colon (;) indicates  
-- the end of a statement or  
-- declaration, while a double  
-- dash (--) indicates a comment.

***std* is a resource library (data types)**

**where we save our design**

**only the *ieee* library must be explicitly written**

# *ieee library*

- *std\_logic\_1164*
  - STD\_LOGIC (8 levels)
  - STD\_ULOGIC (9 levels)
- *std\_logic\_arith*
  - the SIGNED and UNSIGNED data types
  - arithmetic and comparison operations
  - data conversion functions
- *std\_logic\_signed*
- *std\_logic\_unsigned*

# ENTITY

- An ENTITY is a list with specifications of all input and output pins (PORTS) of the circuit.


```
ENTITY entity_name IS  
  PORT (  
    port_name : signal_mode signal_type;  
    port_name : signal_mode signal_type;  
    ...);  
END entity_name;
```

**BIT, STD\_LOGIC, INTEGER, etc.**

**IN, OUT, INOUT, or BUFFER**




# Signal modes

 

**Figure 2.3**  
Signal *modes*.

# Example (For ENTITY)

 

**Figure 2.4**  
NAND gate.

```
ENTITY nand_gate IS  
    PORT (a, b : IN BIT;  
          x : OUT BIT);  
END nand_gate;
```


# ARCHITECTURE

- **An architecture has two parts:**
  - declarative part (optional),
  - code part

```
ARCHITECTURE architecture_name OF entity_name IS  
    [declarations]  
BEGIN  
    (code)  
END architecture_name;
```

[©Hwan08]

# Example (For ARCHITECTURE)

 


**Figure 2.4**  
NAND gate.

```
ENTITY nand_gate IS  
    PORT (a, b : IN BIT;  
          x : OUT BIT);  
END nand_gate;
```

```
ARCHITECTURE myarch OF nand_gate IS  
BEGIN  
    x <= a NAND b;  
END myarch;
```

# Introductory Examples


## 1- DFF with Asynchronous Reset

 

**Figure 2.5**  
DFF with asynchronous reset.

# Introductory Examples ...


## 2 - DFF plus NAND Gate

 

**Figure 2.7**  
DFF plus NAND gate.

# DFF with Asynchronous Reset


```
-----  
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
-----  
ENTITY dff IS  
    PORT ( d, clk, rst: IN STD_LOGIC;  
          q: OUT STD_LOGIC);  
END dff;  
-----
```

 

**Figure 2.5**  
DFF with asynchronous reset.

# DFF with Asynchronous Reset ...

```
-----  
ARCHITECTURE behavior OF dff IS  
BEGIN  
    PROCESS (rst, clk)  
    BEGIN  
        IF (rst='1') THEN  
            q <= '0';  
        ELSIF (clk'EVENT AND clk='1') THEN  
            q <= d;  
        END IF;  
    END PROCESS;  
END behavior;  
-----
```

 


**Figure 2.5**  
DFF with asynchronous reset.

Note: VHDL is not case sensitive.



# DFF with Asynchronous Reset ...

- Simulation result

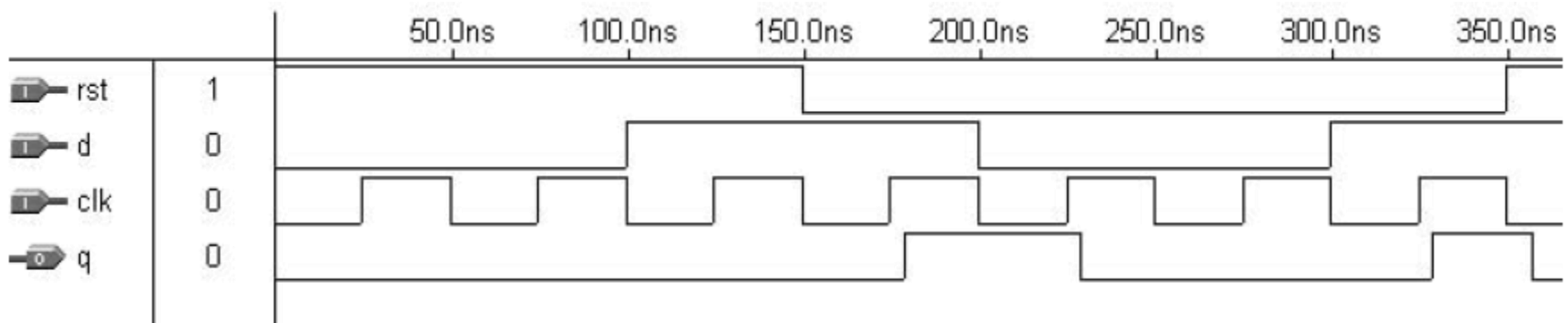


**Figure 2.6**  
Simulation results of example 2.1.

# DFF plus NAND Gate

```
-----  
ENTITY example IS  
  PORT ( a, b, clk: IN BIT;  
         q: OUT BIT);  
END example;  
-----
```


```
ARCHITECTURE example OF example IS  
  SIGNAL temp : BIT;  
BEGIN  
  temp <= a NAND b;  
  PROCESS (clk)  
  BEGIN  
    IF (clk'EVENT AND clk='1') THEN q<=temp;  
    END IF;  
  END PROCESS;  
END example;  
-----
```

 

**Figure 2.7**  
DFF plus NAND gate.

# DFF plus NAND Gate ...

- Simulation result

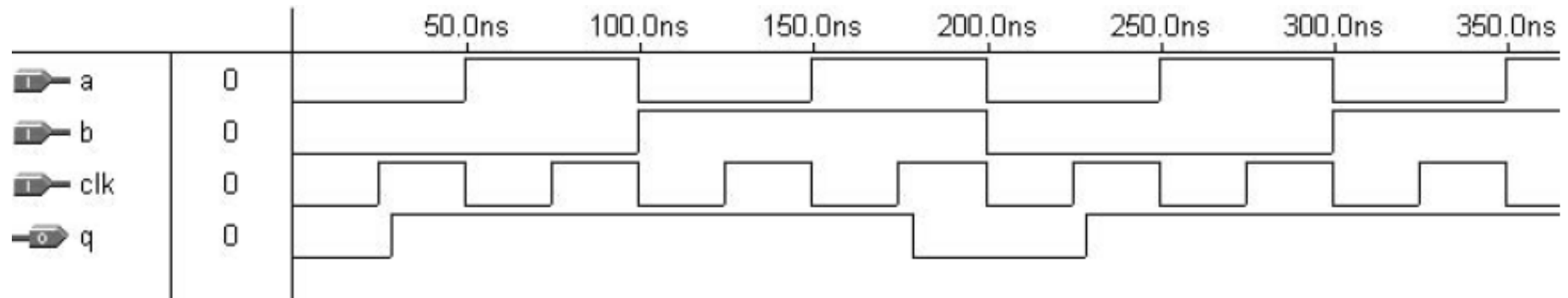

**Figure 2.8**

Simulation results of example 2.2.

# Next session

## 3 Data Types

3.1 Pre-Defined Data Types

3.2 User-Defined Data Types

3.3 Subtypes

3.4 Arrays

3.5 Port Array

3.6 Records

3.7 Signed and Unsigned Data Types

3.8 Data Conversion

3.9 Summary

3.10 Additional Examples