



Circuit Design with VHDL

Chapters 1-3: Introduction

Instructor: Ali Jahanian



Text book & required tools

- Class

- Textbook:



- Volnei A. Pedroni, “Circuit Design with VHDL”, Third Edition, MIT Press, 2020.

- Software:

- ModelSim
 - ISE/Vivado

- Slides’ reference:

- Dr. Saeed Gorgin

  

Evaluation

- **Grades**

- Homework & projects 30% <No delivery= -1/2 grade>
- Quiz 10% <No delivery= -1/2 grade>
- Final Project 10%
- Final Exam 50%


Course Strategy

- At the end of this course you should be able to:
 - Concepts of Hardware Modeling
 - Design and modeling with VHDL
 - Synthesize and implement of digital systems on FPGAs
 - Master on High-Level Synthesis


Course Outline

- Introduction
- Circuit Design with VHDL
- FPGA structure
- Hardware Synthesis using ISE
- High-level Synthesis

Moore's Law



 


50 Years of Moore's law

 


Design Styles

   - Full-custom design
- Semi-custom design
- Gate array design



ASIC or FPGA?

FPGA VS ASIC Comparison

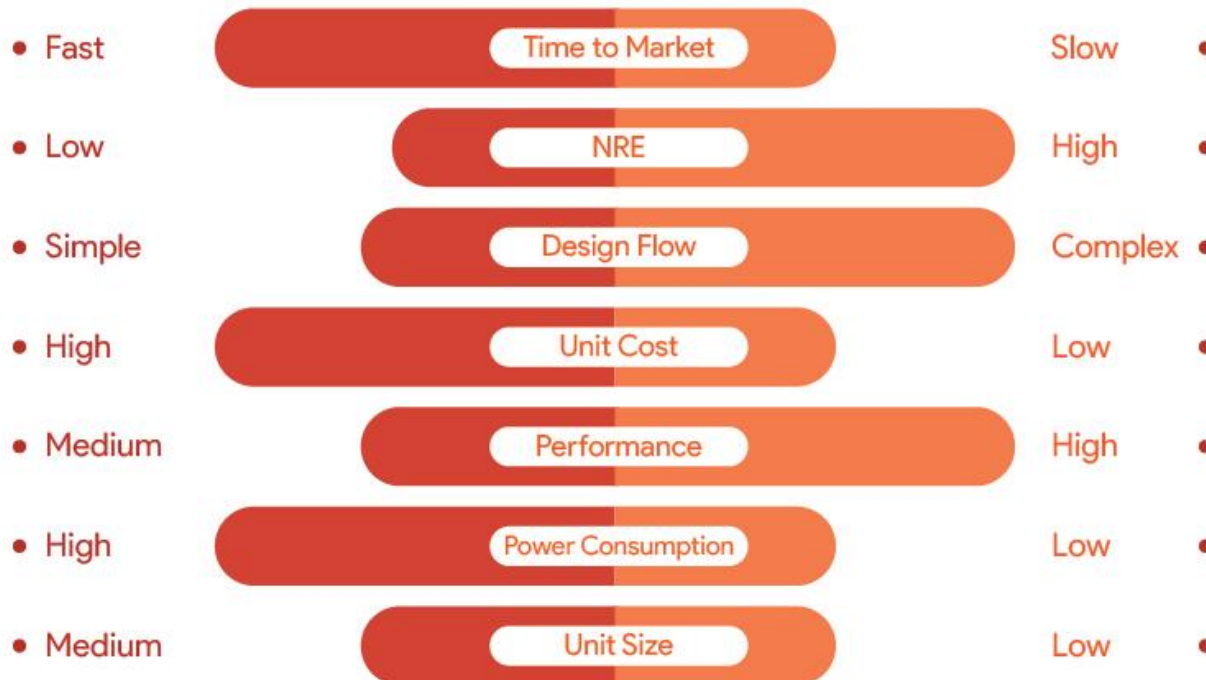

HARDWAREBEE

Basic Logic Review

- Combinational Logic Review [©Hwan08]
 - Basic Logic Review
 - Basic Gates (AND,OR,XOR,NAND,NOR)
 - DeMorgan's Law
 - Combinational Logic Blocks
 - Multiplexers
 - Decoders, Demultiplexers
 - Encoders, Priority Encoders
 - Half Adders, Full Adders
 - Multi-Bit Combinational Logic Blocks
 - Multi-bit multiplexers
 - Multi-bit adders
 - Comparators

Basic Logic Review

- Sequential Logic Review [©Hwan08]
 - Sequential Logic Building Blocks
 - Latches, Flip-Flops
 - Sequential Logic Circuits
 - Registers, Shift Registers, Counters
 - Memory (RAM, ROM)
 - Simple Finite State Machines (Mealy, Moore)

Basic Logic Review

- Digital Logic
 - Digital logic gates implement Boolean functions
 - 1 represents true
 - 0 represent false
 - Two types of logic
 - Combinational logic: output depends on the input
 - Sequential logic: output depends on the input and previous outputs and/or inputs


Digital Logic

- Digital logic gates implement Boolean functions
 - 1 represents true
 - 0 represent false
- Two types of logic
 - Combinational logic: output depends on the input
 - Sequential logic: output depends on the input and previous outputs and/or inputs

Basic Concepts

- Simple logic gates
 - AND \rightarrow 0 if one or more inputs is 0
 - OR \rightarrow 1 if one or more inputs is 1
 - NOT
 - NAND = AND + NOT
 - 1 if one or more inputs is 0
 - NOR = OR + NOT
 - 0 if one or more input is 1
 - XOR implements exclusive-OR function
- NAND and NOR gates require fewer transistors than AND and OR in standard CMOS
- Functionality can be expressed by a truth table
 - A truth table lists output for each possible input combination

Basic Logic Gates

 


AND gate

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1



OR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

 


NOT gate

A	F
0	1
1	0


Logic symbol

Truth table

 

NAND gate

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

 

NOR gate

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0



XOR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

Logic symbol

Truth table

Number of Functions


- Number of functions
 - With N logical variables, we can define 2^{2^N} functions
 - Some of them are useful
 - AND, NAND, NOR, XOR, ...
 - Some are not useful:
 - Output is always 1
 - Output is always 0

Complete Set of Gates


- Complete sets
 - A set of gates is complete
 - if we can implement any logical function using only the type of gates in the set
 - Some example complete sets
 - {AND, OR, NOT}
 - {AND, NOT}
 - {OR, NOT}
 - {NAND}
 - {NOR}
 - Minimal complete set
 - A complete set with no redundant elements.

NAND as a Complete Set


- Proving NAND gate is universal

 

AND gate

 

NOT gate

 


OR gate

Logic Functions

- Logical functions can be expressed in several ways:
 - Truth table
 - Logical expressions
 - Graphical form
 - HDL code
- Example:
 - Majority function
 - Output is one whenever majority of inputs is 1
 - We use 3-input majority function

Logic Functions...

 - Truth table
- Logical expression form
 $F = A B + B C + A C$
- Graphical schematic form



A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Boolean Algebra

Boolean identities

Name	AND version	OR version
Identity	$x \cdot 1 = x$	$x + 0 = x$
Complement	$x \cdot x' = 0$	$x + x' = 1$
Commutative	$x \cdot y = y \cdot x$	$x + y = y + x$
Distribution	$x \cdot (y + z) = xy + xz$	$x + (y \cdot z) = (x + y)(x + z)$
Idempotent	$x \cdot x = x$	$x + x = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$

Boolean Algebra...

- Boolean identities (cont'd)

Name	AND version	OR version
Involution	$x = (x')'$	
Absorption	$x \cdot (x + y) = x$	$x + (x \cdot y) = x$
Associative	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x + (y + z) = (x + y) + z$
de Morgan	$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$
(de Morgan's law in particular is very useful)		

Majority Function Using Other Gates

- Using NAND gates

- Get an equivalent expression

$$A B + C D = (A B + C D)''$$

- Using de Morgan's law

$$A B + C D = ((A B)' \cdot (C D)')'$$


- Can be generalized

- Example: Majority function


$$A B + B C + A C = ((A B)' \cdot (B C)' \cdot (A C)')'$$

Majority Function Using Other Gates...

- Majority function

 


Combinational Logic Building Blocks

 

- Multiplexers

- n binary inputs (binary input = 1-bit input)
- $\log_2 n$ binary selection inputs
- 1 binary output
- Function: one of n inputs is placed onto output
- Called **n-to-1** multiplexer


2-to-1 Multiplexer

 


(a) Graphical symbol

s	f
0	w_0
1	w_1

(b) Truth table

 


(c) Sum-of-products circuit

 

(d) Circuit with transmission gates


4-to-1 Multiplexer

 

(a) Graphic symbol


s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

 

(c) Circuit

Decoders

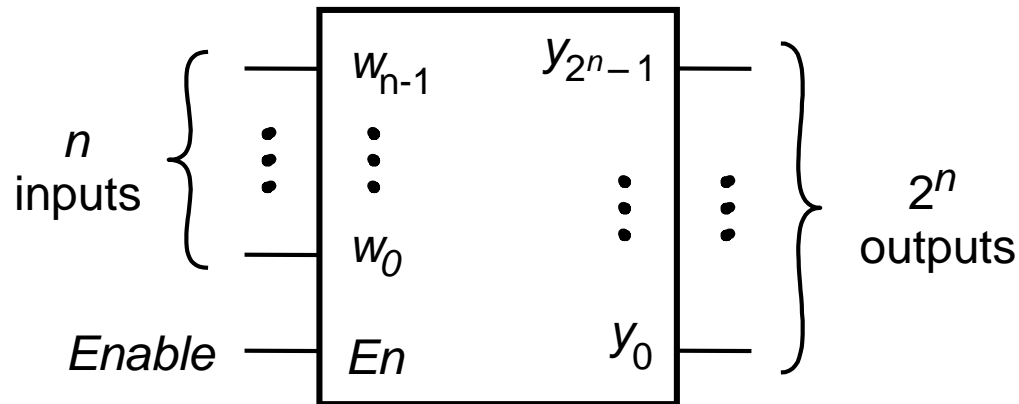


- **Decoder**
 - n binary inputs
 - 2^n binary outputs
 - Function: decode encoded information
 - If enable=1, one output is asserted high, the other outputs are asserted low
 - If enable=0, all outputs asserted low
 - Often, enable pin is not needed (i.e. the decoder is always enabled)
 - Called **n-to-2ⁿ** decoder
 - Can consider n binary inputs as a single n -bit input
 - Can consider 2^n binary outputs as a single 2^n -bit output
 - Decoders are often used for RAM/ROM addressing


2-to-4 Decoder

En	w_1	w_0	y_3	y_2	y_1	y_0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	-	-	0	0	0	0

(a) Truth table

 


(b) Graphical symbol

 


(c) Logic circuit

Demultiplexers

 


- Demultiplexer
 - 1 binary input
 - n binary outputs
 - $\log_2 n$ binary selection inputs
 - Function: places input onto one of n outputs, with the remaining outputs asserted low
 - Called **1-to- n** demultiplexer
- Closely related to decoder
 - Can build 1-to- n demultiplexer from $\log_2 n$ -to- n decoder by using the decoder's enable signal as the demultiplexer's input signal, and using decoder's input signals as the demultiplexer's selection input signals.

1-to-4 Demultiplexer

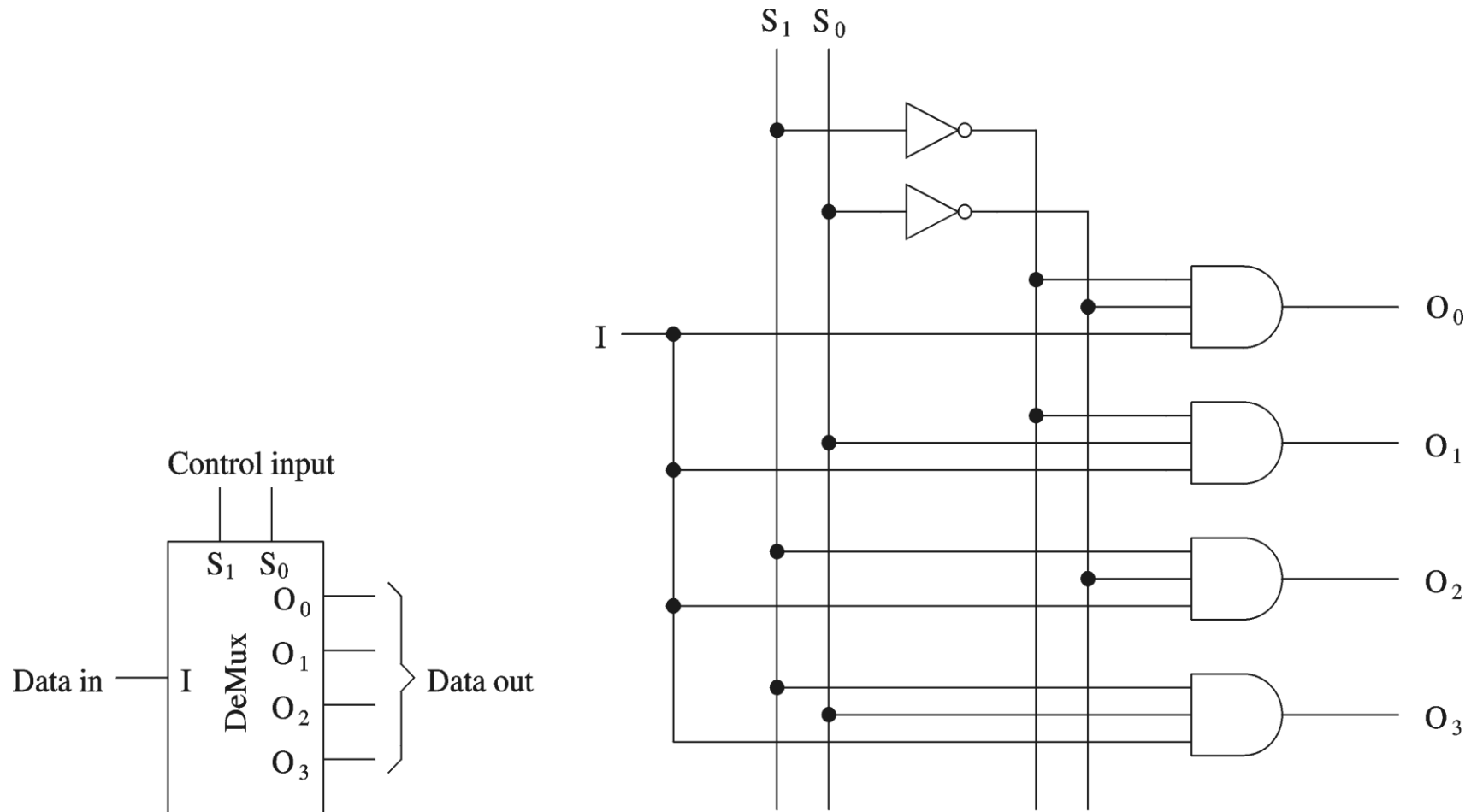

Encoders

 


- Encoder
 - 2ⁿ binary inputs
 - n binary outputs
 - Function: encodes information into an n-bit code
 - Called **2ⁿ-to-n** encoder
 - Can consider 2ⁿ binary inputs as a single 2ⁿ-bit input
 - Can consider n binary output as a single n-bit output
- Encoders only work when **exactly one** binary input is equal to 1

4-to-2 Encoder


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Truth table

 

(b) Circuit

Priority Encoders

 

- Priority Encoder
 - 2^n binary inputs
 - n binary outputs
 - 1 binary "valid" output
 - Function: encodes information into an n -bit code based on priority of inputs
 - Called **2^n -to- n** priority encoder
- Priority encoder allows for multiple inputs to have a value of '1', as it encodes the input with the highest priority (MSB = highest priority, LSB = lowest priority)
 - "valid" output indicates when priority encoder output is valid
 - Priority encoder is more common than an encoder

4-to-2 Priority Encoder


w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	-	-	0
0	0	0	1	0	0	1
0	0	1	-	0	1	1
0	1	-	-	1	0	1
1	-	-	-	1	1	1

Single-Bit Adders

- Half-adder
 - Adds two binary (i.e. 1-bit) inputs A and B
 - Produces a *sum* and *carryout*
 - Problem: Cannot use it alone to build larger adders
- Full-adder
 - Adds three binary (i.e. 1-bit) inputs A , B , and *carryin*
 - Like half-adder, produces a *sum* and *carryout*
 - Allows building M-bit adders ($M > 1$)
 - Simple technique
 - Connect C_{out} of one adder to C_{in} of the next
 - These are called *ripple-carry adders*
 - Shown in next section


Single-Bit Adders ...

A	B	Sum	C _{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 


(a) Half-adder truth table and implementation

A	B	C _{in}	Sum	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

(b) Full-adder truth table and implementation

Multi-bit 4-to-1 Multiplexer

 


(a) Graphic symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

- When drawing schematics, can draw **multi-bit** multiplexers
- Example: 4-to-1 (8 bit) multiplexer
 - 4 inputs (each 8 bits)
 - 1 output (8 bits)
 - 2 selection bits
- Can also have multi-bit 2-to-1 muxes, 16-to-1 muxes, etc.


4-to-1 (8-bit) Multiplexer

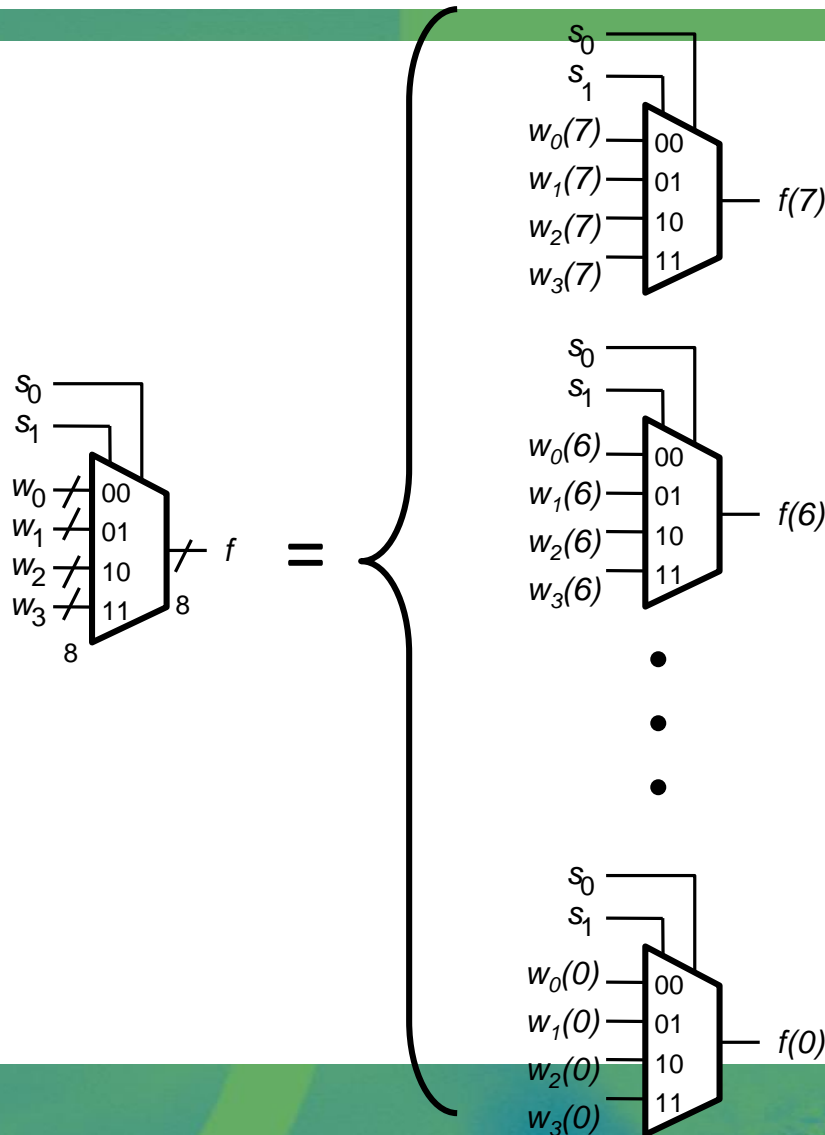

A 4-to-1 (8-bit) multiplexer is composed of eight 4-to-1 (1-bit) multiplexers


Multi-Bit Ripple-Carry Adder

 - A 16-bit ripple-carry adder is composed of 16 (1-bit) full adders
 - Inputs: 16-bit A, 16-bit B, 1-bit carryin (set to zero in the figure below)
 - Outputs: 16-bit sum R, 1-bit overflow




Comparator

 - Used to compare two M-bit numbers and produce a flag ($M > 1$)
 - Inputs: M-bit input A, M-bit input B
 - Output: 1-bit output flag
 - 1 indicates condition is met
 - 0 indicates condition is not met
 - Can compare: $>$, \geq , $<$, \leq , $=$, etc.




Example: 4-bit comparator (A = B)

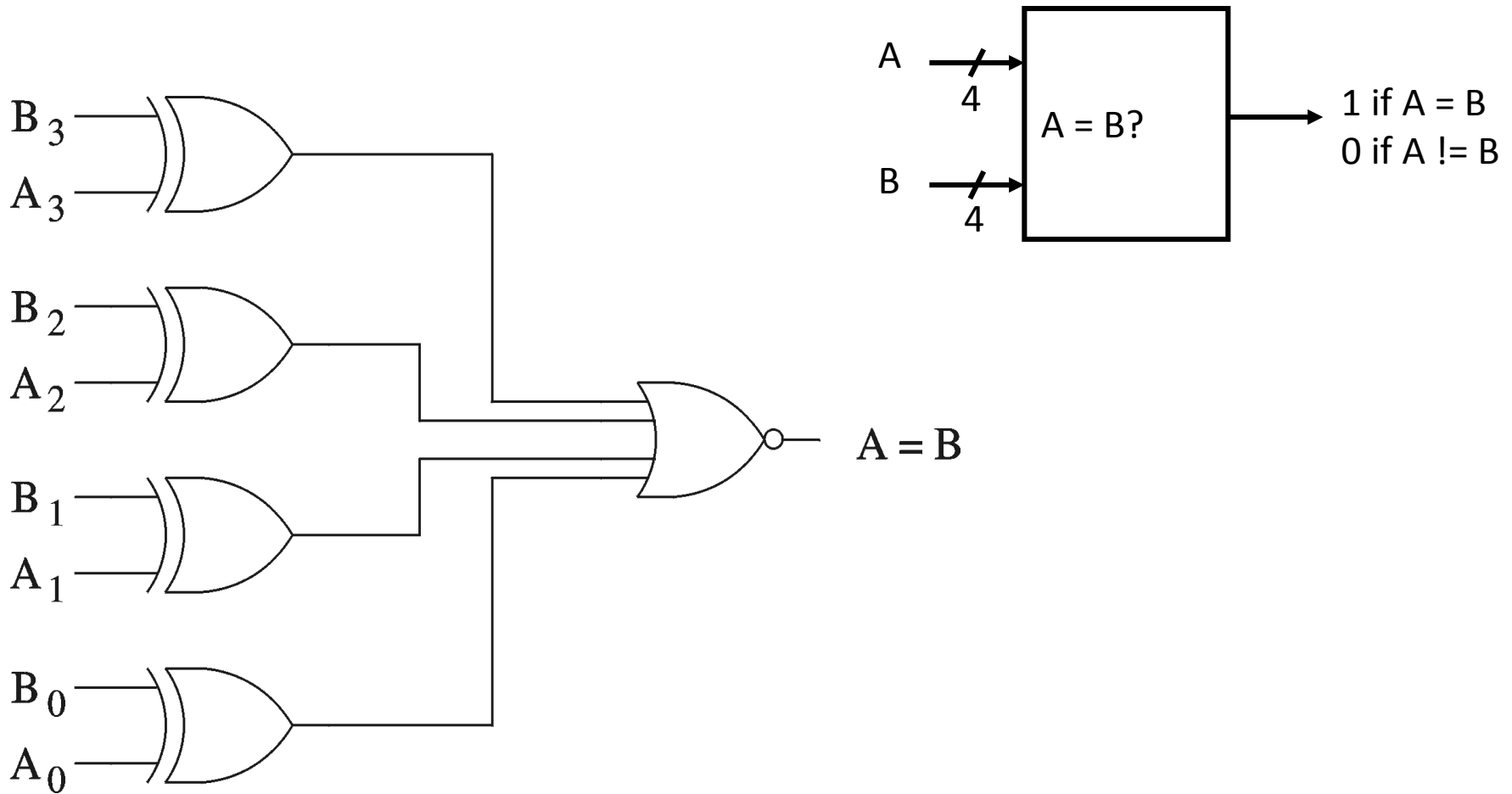

Combinational Logic Example: ALU (1-bit)

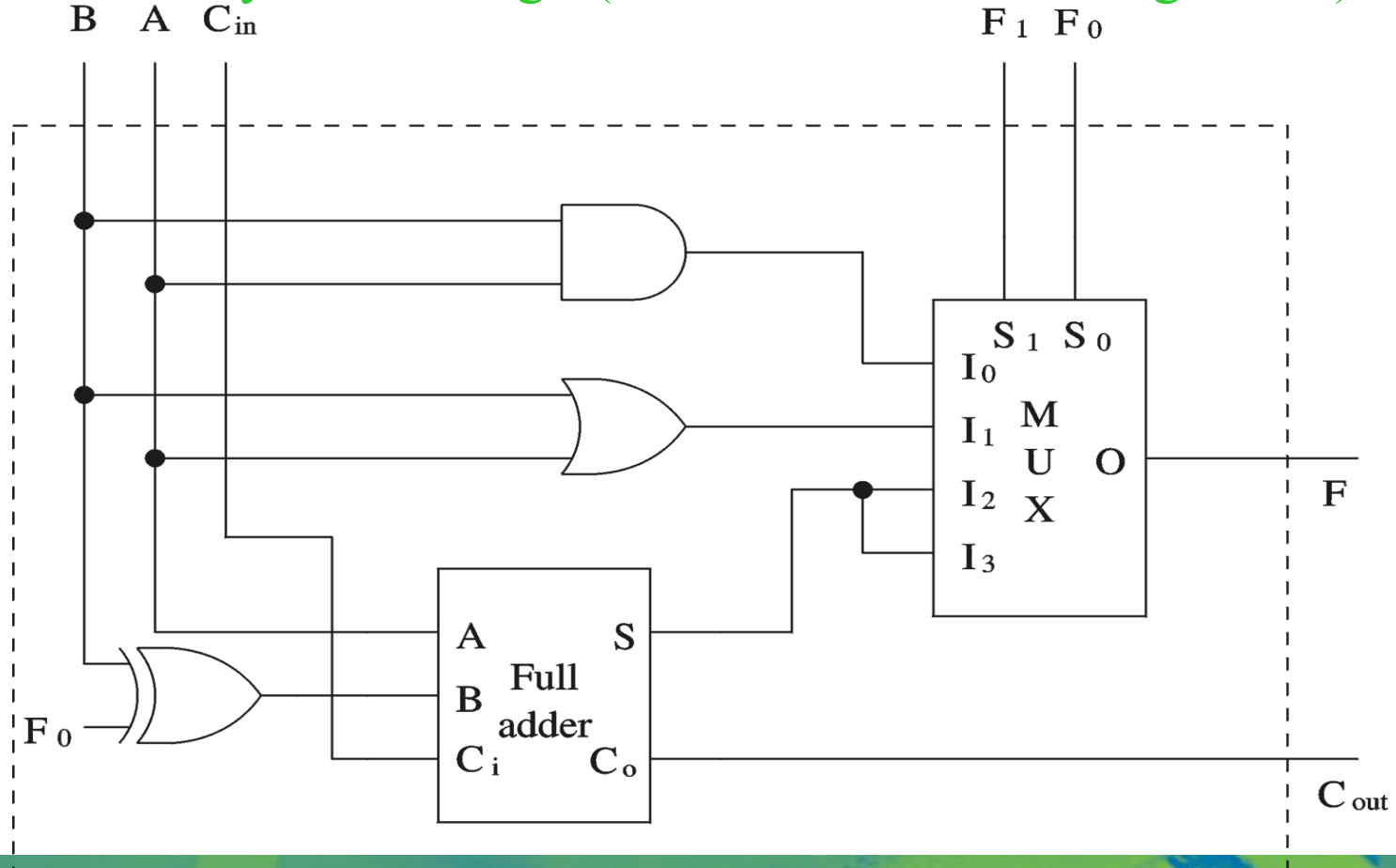- Preliminary ALU design (ALU = arithmetic + logic unit)



Sequential Logic Review

- Sequential Logic Building Blocks
 - Latches, Flip-Flops
- Sequential Logic Circuits
 - Registers, Shift Registers, Counters
 - Memory (RAM, ROM)
 - Simple Finite State Machines (Mealy, Moore)


Introduction to Sequential Logic

- Output depends on current as well as past inputs
 - Depends on the history
 - Have “memory” property
- Sequential circuit consists of
 - Combinational circuit
 - Feedback circuit
 - Past input is encoded into a set of state variables
 - Uses feedback (to feed the state variables)
 - Simple feedback
 - Uses flip flops

Introduction ...

- Main components of a typical synchronous sequential circuit


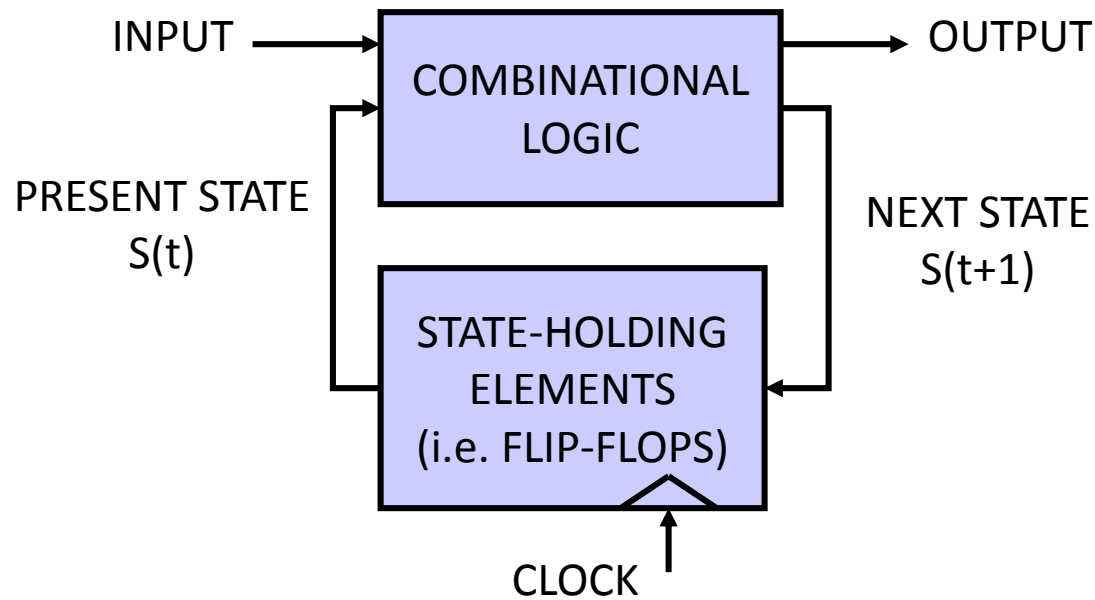
(synchronous = uses a clock to keep circuits in lock step)





State-Holding Memory Elements

- Latch versus Flip Flop
 - Latches are level-sensitive: whenever clock is high, latch is transparent
 - Flip-flops are edge-sensitive: data passes through (i.e. data is sampled) only on a rising (or falling) edge of the clock
 - Latches cheaper to implement than flip-flops
 - Flip-flops are easier to design with than latches

D Latch vs. D Flip-Flop

  


Latch transparent when clock is high

  


"Samples" D on rising edge of clock

D Flip-Flop (positive edge triggered)

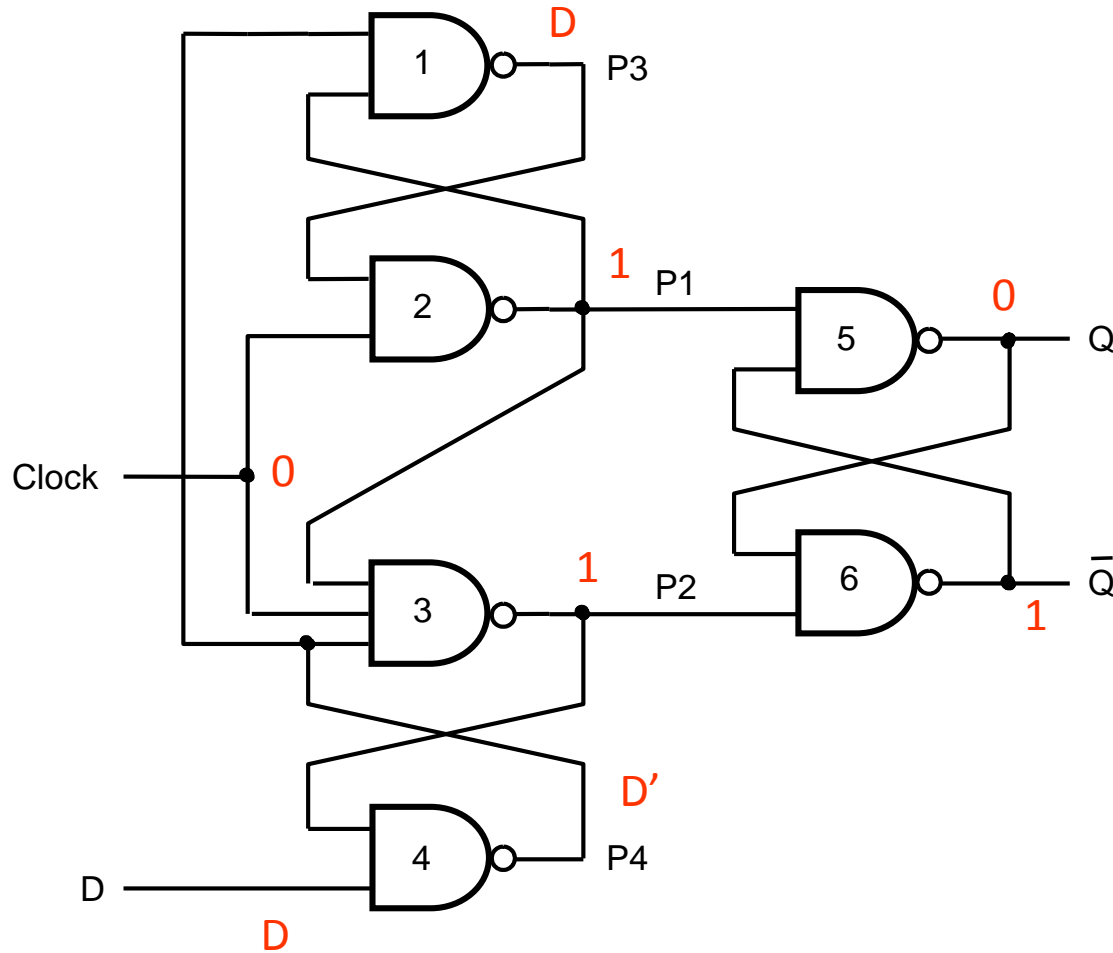


(a) Circuit

 


(b) Graphical symbol

D Flip-Flop (positive edge triggered)

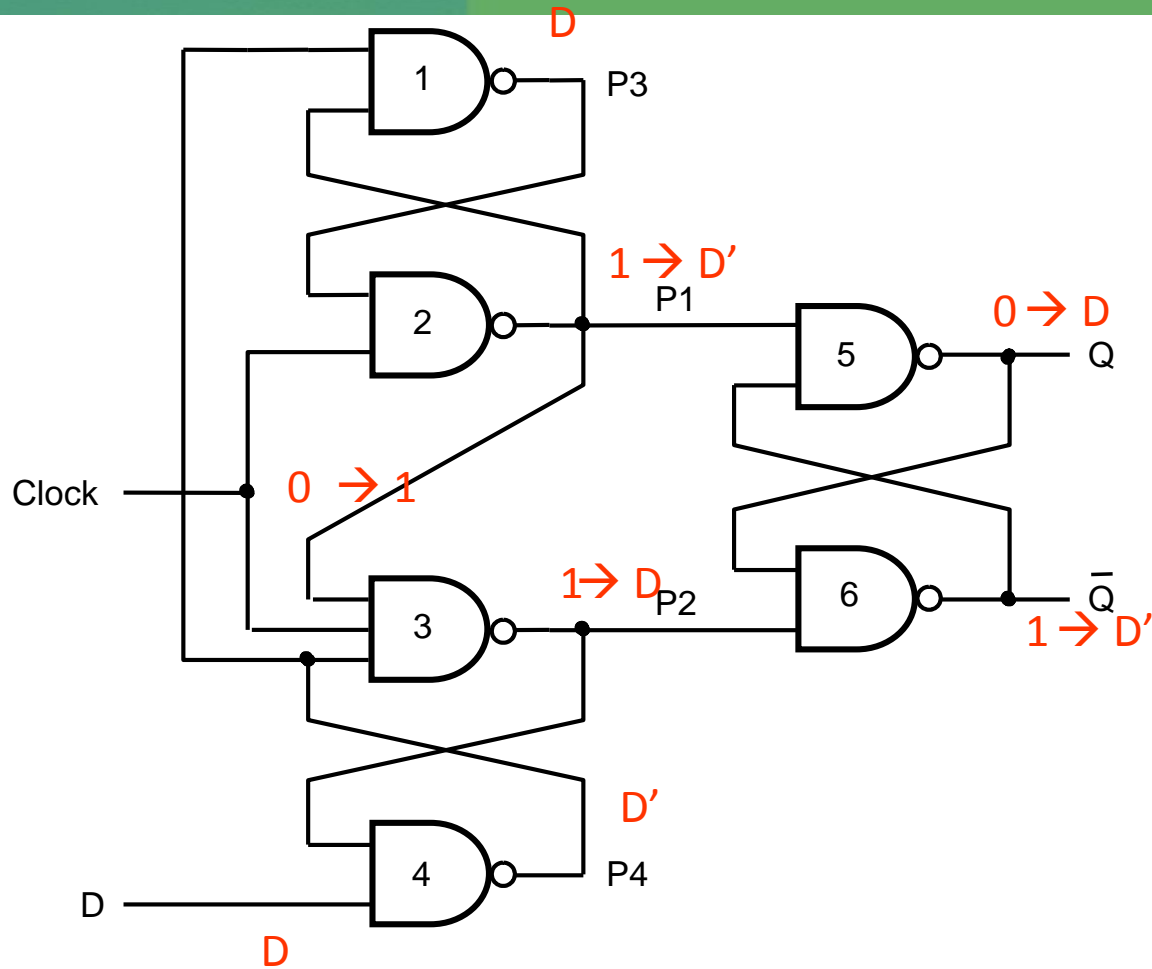


(a) Circuit

 

 
(b) Graphical symbol

D Flip-Flop with Asynchronous Preset and Clear

- Bubble on the symbol means “active-low”
 - When preset = 0, preset Q to 1
 - When preset = 1, do nothing
 - When clear = 0, clear Q to 0
 - When clear = 1, do nothing
- “Preset” and “Clear” also known as “Set” and “Reset” respectively
- In this circuit, preset and clear are asynchronous
 - Q changes immediately when preset or clear are active, regardless of clock




(a) Circuit

 

(b) Graphical symbol


D Flip-Flop with Synchronous Clear

 

- Asynchronous active-low clear: Q immediately clears to 0
- Synchronous active-low clear: Q clears to 0 on rising-edge of clock


Other Types of Flip-Flops

D Flip-Flop

 


D	Q(t+1)
0	0
1	1

Set-Reset (SR) Flip-Flop

 


S	R	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	not allowed

Toggle (T) Flip-Flop

 

T	Q(t+1)
0	Q(t)
1	$\overline{Q(t)}$

JK Flip-Flop

 


J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\overline{Q(t)}$


Sequential Logic Circuits

- Register

 - In typical nomenclature, a register is a name for a collection of flip-flops used to hold a bus (i.e. `std_logic_vector`)



Shift Register


 


(a) Circuit



	In	Q_1	Q_2	Q_3	$Q_4 = \text{Out}$
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1

(b) A sample sequence

Parallel Access Shift Register

 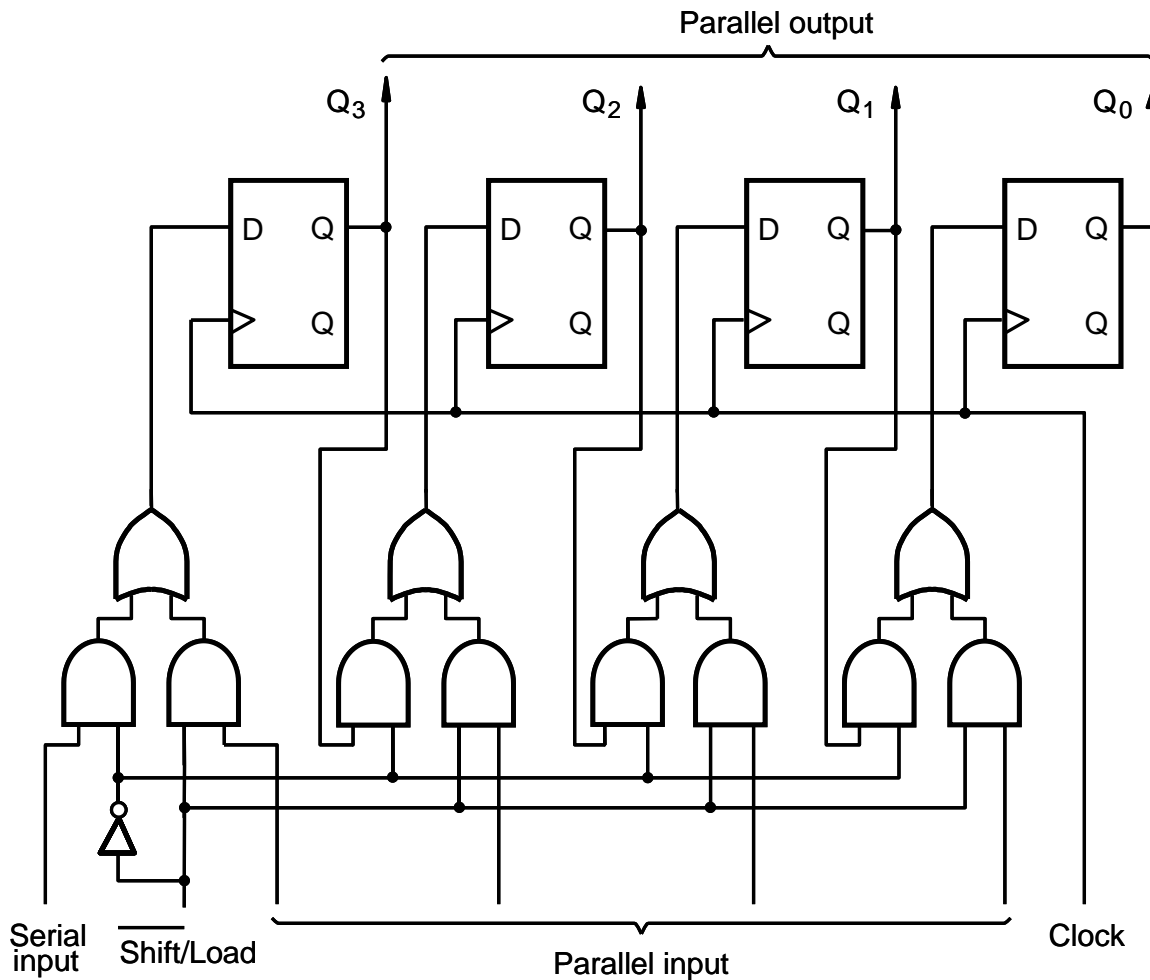


Synchronous Up Counter

  


- Enable (synchronous): when high enables the counter, when low counter holds its value
- Load (synchronous) : when load = 1, load the desired value into the counter
- Output carry: indicates when the counter “rolls over”
- D3 down to D0, Q3 down to Q0 is how to interpret MSB to LSB

Memories (Random Access Memory)

- More efficient than registers for storing large amounts of data
- Can read and write to RAM
- Addressable memory
- Can be synchronous (with clock) or asynchronous (no clock)
- SRAM dimensions are:
 - (number of words) x (bits per word) SRAM
- Address is m bits, data is n bits
 - $2^m \times n$ -bit RAM
- Example: address is 5 bits, data is 8 bits
 - 32×8 -bit RAM
- Write
 - Data_in and address are stable
 - Assert write signal (then de-assert)
- Read
 - Address is stable
 - Assert read signal
 - Data_out is valid

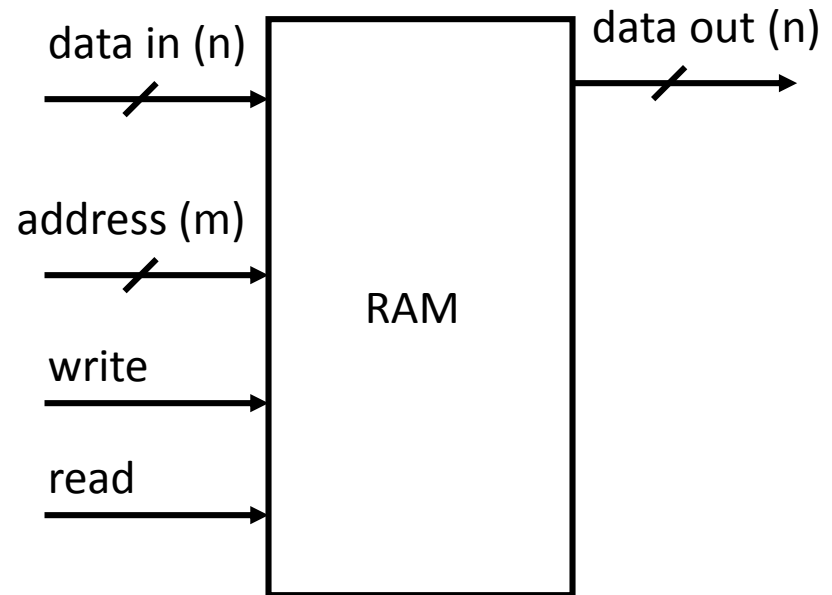


Random Access Memory (RAM) ...

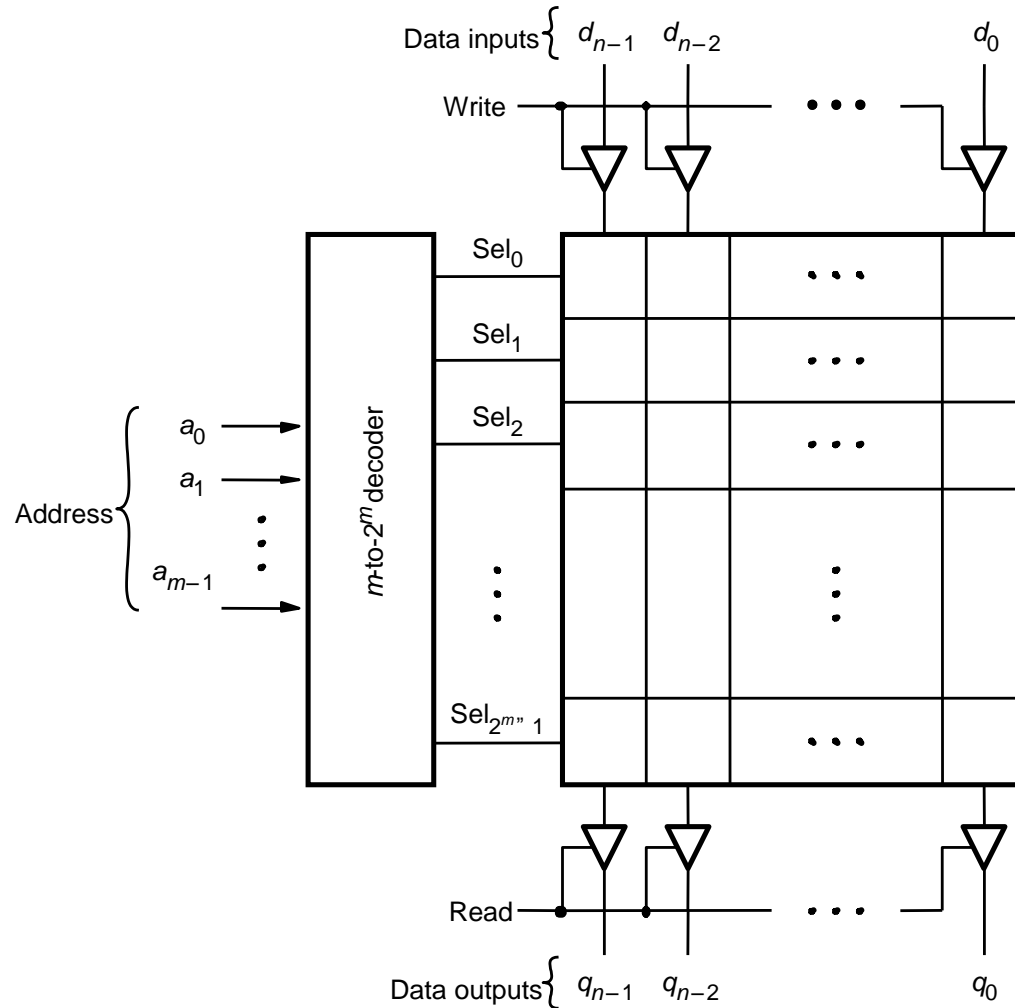


Read Only Memory (ROM)

 - Similar to RAM except read only
- Addressable memory
- Can be synchronous (with clock) or asynchronous (no clock)



Read-Only Memory (ROM) ...

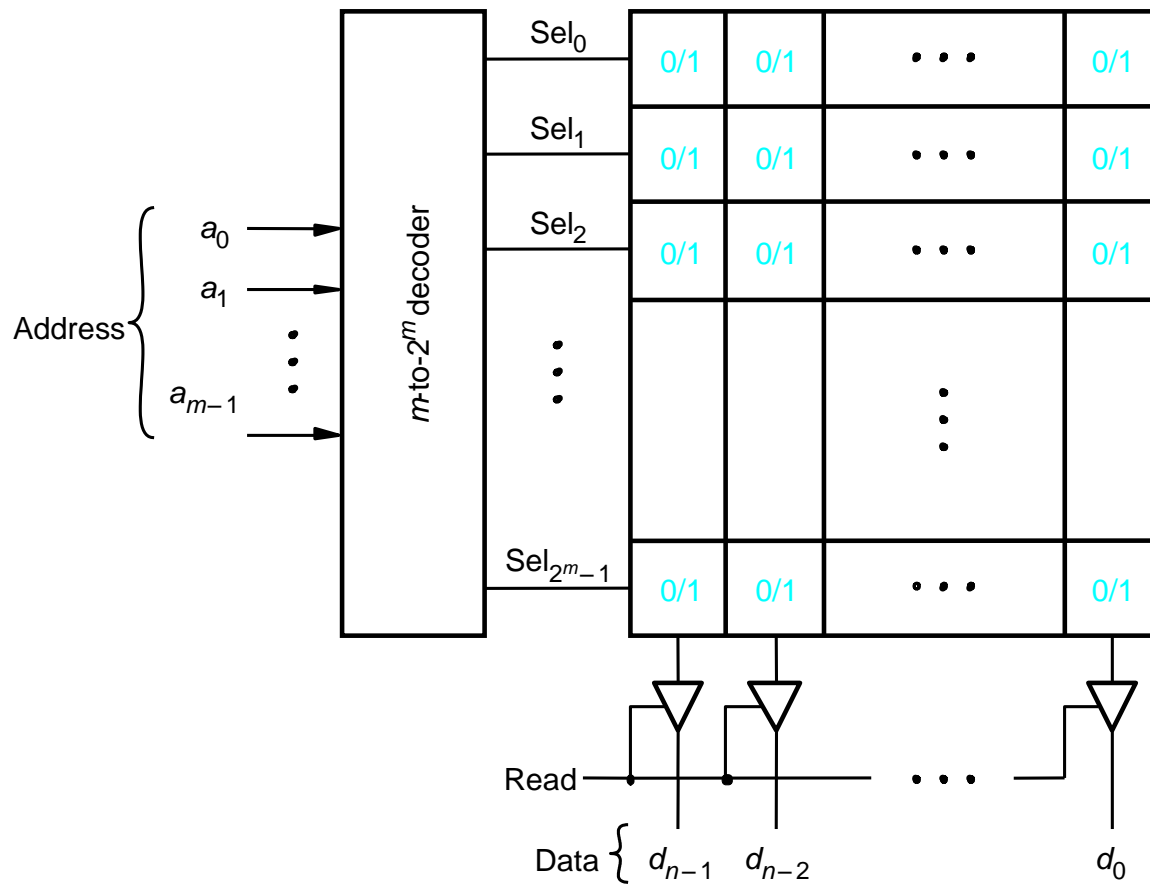

Finite State Machines (FSMs)


- Any Circuit with Memory Is a Finite State Machine
 - Even computers can be viewed as huge FSMs
- Design of FSMs Involves
 - Defining states
 - Defining transitions between states
 - Optimization / minimization
- Above Approach Is Practical for Simple FSMs Only

Mealy vs. Moore State Machines

- Finite State Machines (FSM) are of two types:
- Moore Machines
 - Next State = Function(Input, Present State)
 - Output = Function(Present State)
- Mealy Machines
 - Next State = Function(Input, Present State)
 - Output = Function(Input, Present State)


Moore FSM

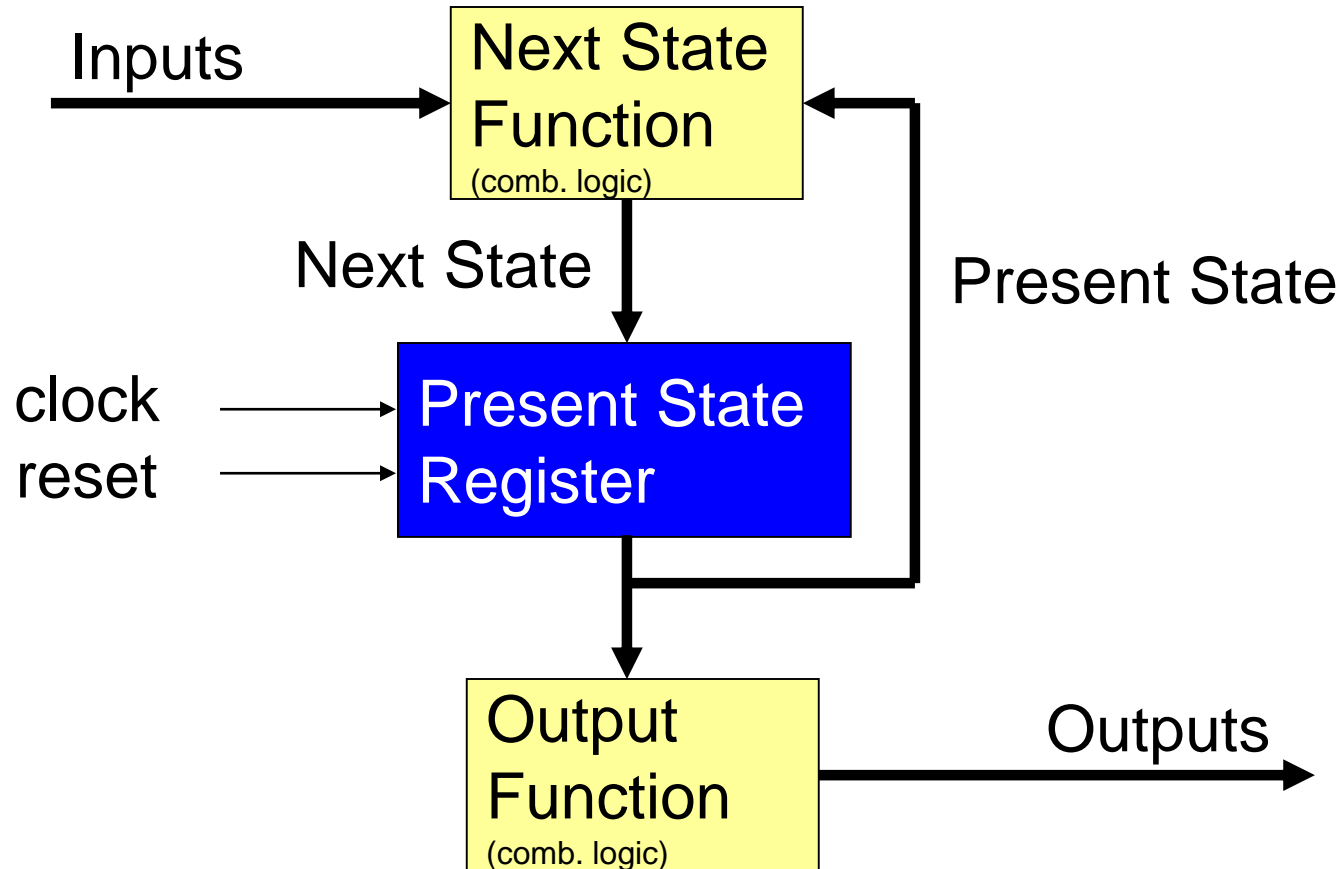- Output Is a Function of a Present State Only




Mealy FSM

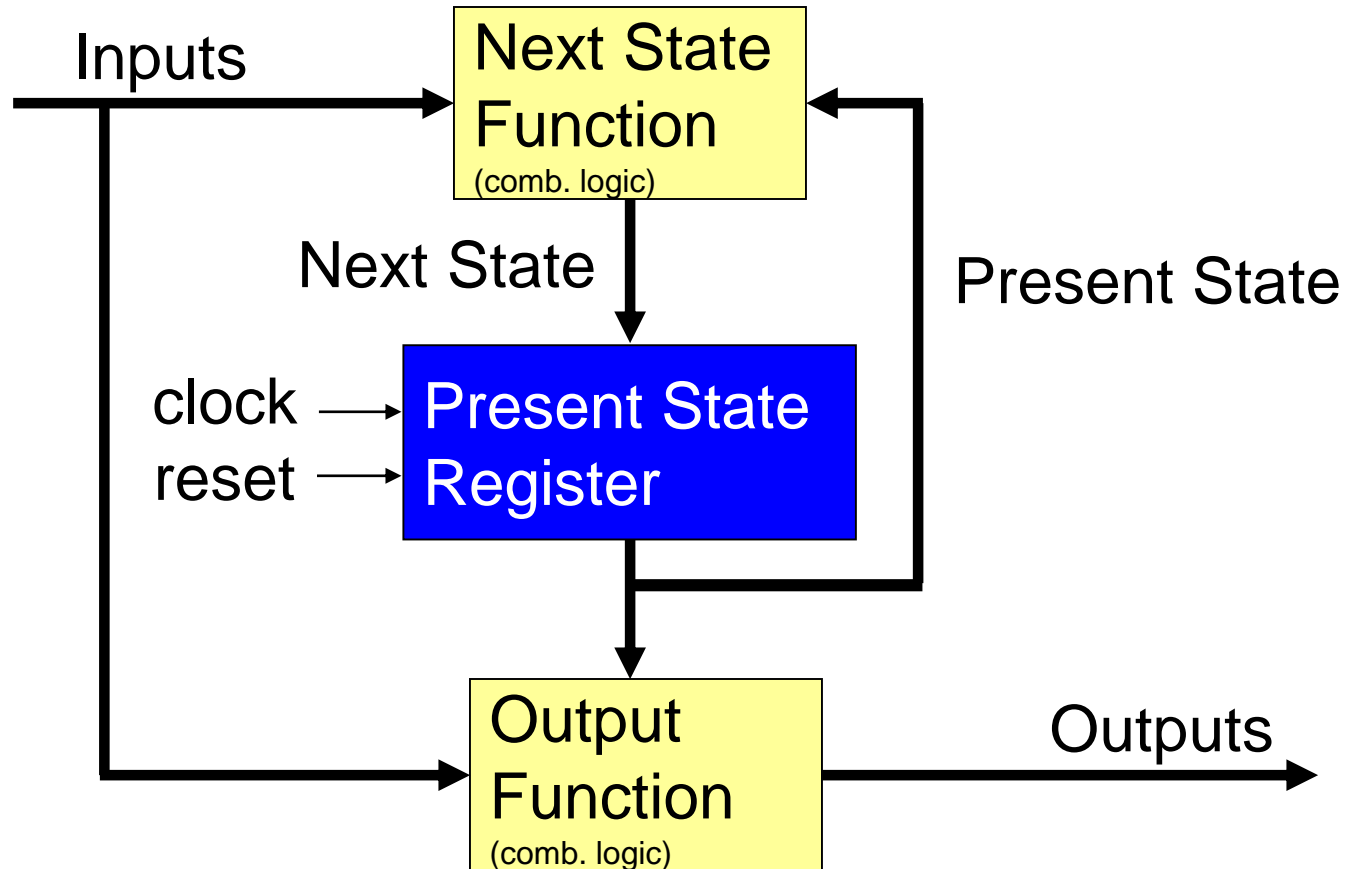
- Output Is a Function of a Present State and Inputs



Moore Machine

 

Mealy Machine

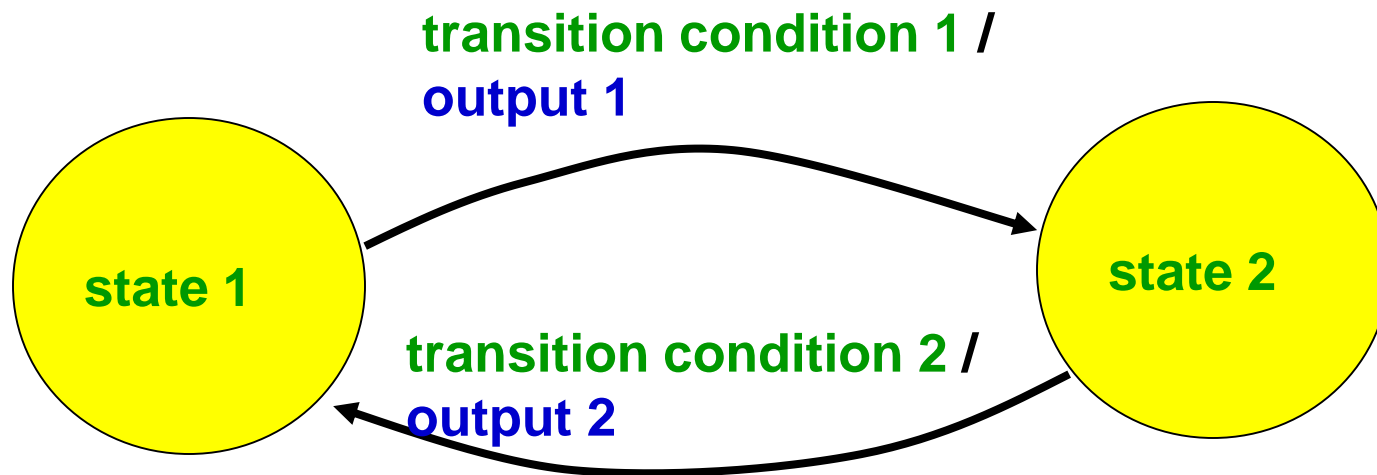

Moore vs. Mealy FSM (1)


- Moore and Mealy FSMs can be functionally equivalent
 - Equivalent Mealy FSM can be derived from Moore FSM and vice versa
- Mealy FSM Has Richer Description and Usually Requires Smaller Number of States
 - Smaller circuit area

Moore vs. Mealy FSM (2)

- Mealy FSM computes outputs as soon as inputs change
 - Mealy FSM responds one clock cycle sooner than equivalent Moore FSM
- Moore FSM Has no combinational path between inputs and outputs
 - Moore FSM is more likely to have a shorter critical path
 - Moore outputs synchronized with clock; Mealy outputs may not be (may have race conditions, timing issues, etc.)

Moore FSM - Example 1

 
- Moore FSM that Recognizes Sequence “10”



Meaning	S0: No	S1: “1”	S2: “10”
of states:	elements	observed	observed
	of the		
	sequence		
	observed		


Mealy FSM - Example 1

 - Mealy FSM that Recognizes Sequence “10”



Meaning of states:	S0: No elements of the sequence observed	S1: “1” observed
-----------------------	--	---------------------

Moore & Mealy FSMs – Example 1

 

FSM Limitations

- Simple finite state machines (those expressed using state diagrams and state tables) good only for simple designs
 - Many inputs and many outputs make it awkward to draw state machines
 - Often only one input affects the next change of state
 - Most outputs remain the same from state to state
- Instead use algorithmic state machines (ASM)

Next Session

- I-CIRCUIT DESIGN

- 1 Introduction

- 1.1 About VHDL

- 1.2 Design Flow

- 1.3 EDA Tools

- 1.4 Translation of VHDL Code into a Circuit

- 1.5 Design Examples